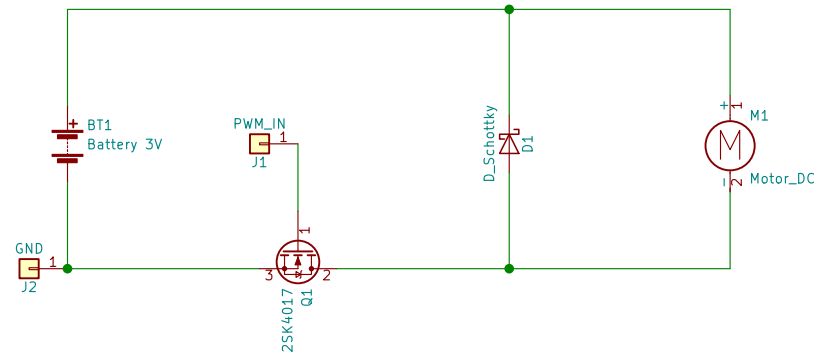


- * Connect PWM_IN (J1) with GPIO 12 or 13 of Raspberry Pi (RasPi).
RasPi's GPIO pins are driven with 3.3 volts. Don't apply 5 volts to PWM_IN (J1).
- * Connect GND (J2) with any ground pin of RasPi.
- * Q1 is a N-channel power MOSFET (enhancement mode).
I used 2SK4017. Equivalentents are needed to have enough drain current,
on 3.3 volts of gate-source voltage.
- * In this schematic, DC motor's (M1) voltage range should be 1.5 volts to 3.0 volts,
and the normal voltage should be 3.0 volts.
M1 is driven with 3.0 volts battery (2 of AA cells).
- * M1 has enough inductance to make a low-pass filter,
so you don't need another coil in series and a capacitor in parallel.
- * Schottky diode's (D1) maximum average forward rectified current
needs enough value compared to current consumption of a DC motor.
For example, current consumption of a DC motor is 650 milliamperes,
and a schottky diode you apply needs 650 milliamperes tolerance for its forward current.
So the value, 1 ampere, is suitable as the diode's maximum average forward rectified current.



A MOSFET has stronger negative feedback than a bipolar transistor. To hide this effect place Q1 like this.

This schematic is exempt from warranty, responsibility,
and liability from any kind and any damage.

Copyright © 2018 Kenta Ishii. All Rights Reserved.

JimmyKenMerchant

Sheet: /

File: dc_motor_driver.sch

Title: DC Motor Driver with Buck (Step-down) Converter

Size: A4 Date: 2019-01-08

KiCad E.D.A. kicad 4.0.7

Rev: 1.0.0

Id: 1/1